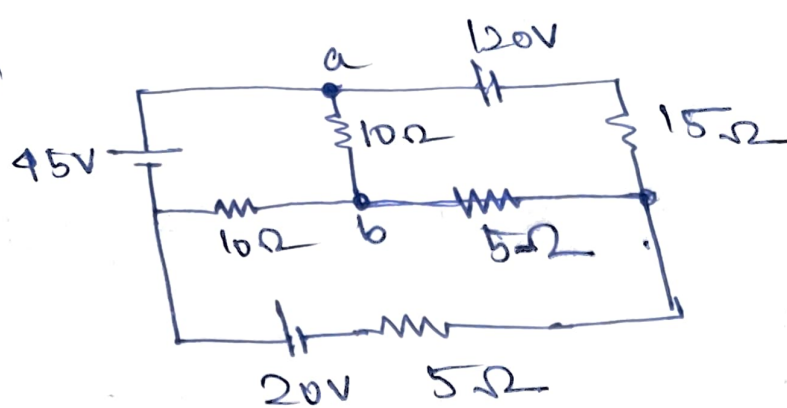



①



(1) Find current through ab branch by applying thevenin's theorem.

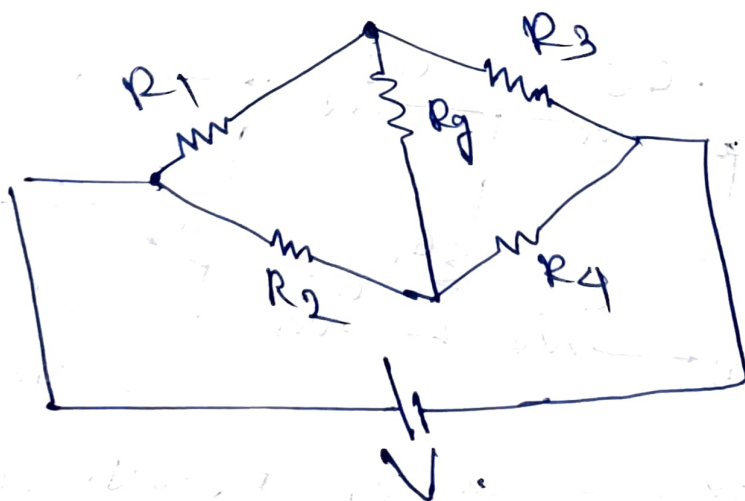
(2) From Thevenin equivalent circuit find the corresponding Norton equivalent circuit.

② Consider the following Wheatstone bridge circuit and derive the condition for balanced Wheatstone Bridge by applying Thevenin's theorem.



③

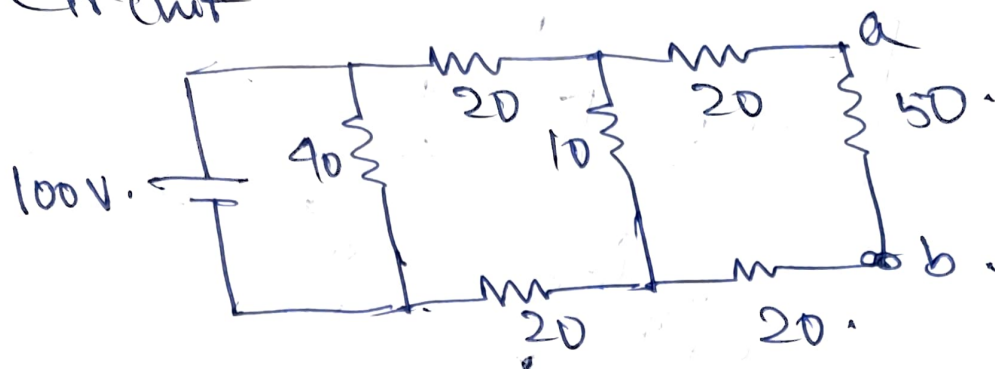
③ Calculate the power which would be dissipated in the $50\ \Omega$ in following circuit.



① Do this problem by applying Kirchhoff's law


② Also by ~~the~~ applying Thevenin's theorem.

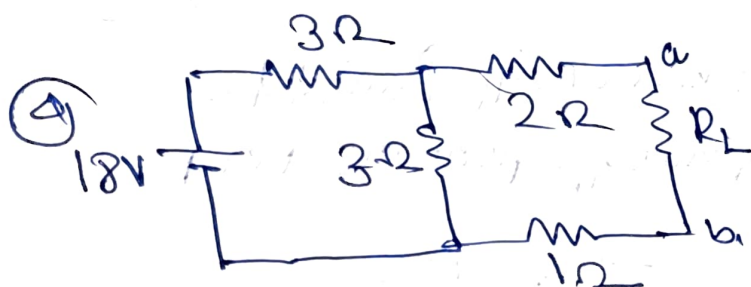③ Determine for which value of load the maximum power will dissipate. Assume that the load is connected between a and b. (See the ~~circuit~~ above figure.).




Find the value of R_L such that ~~Source~~ maximum power is delivered to it.

Also find the maximum value of power.

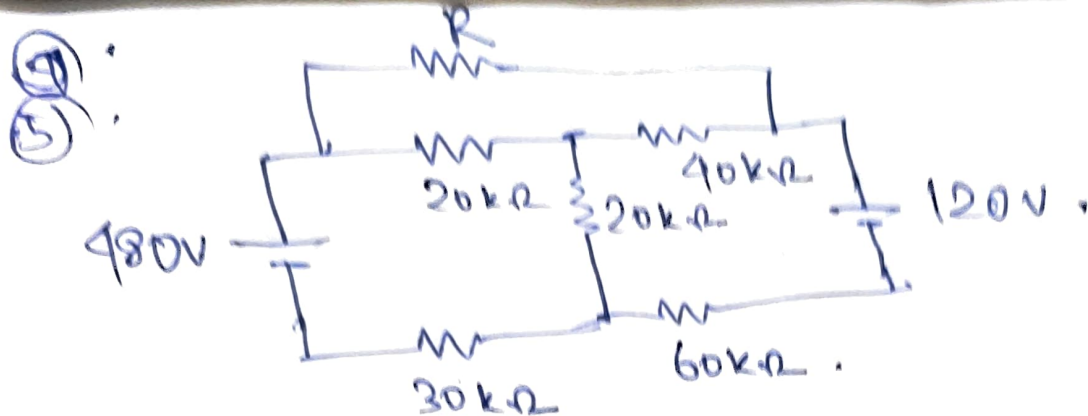

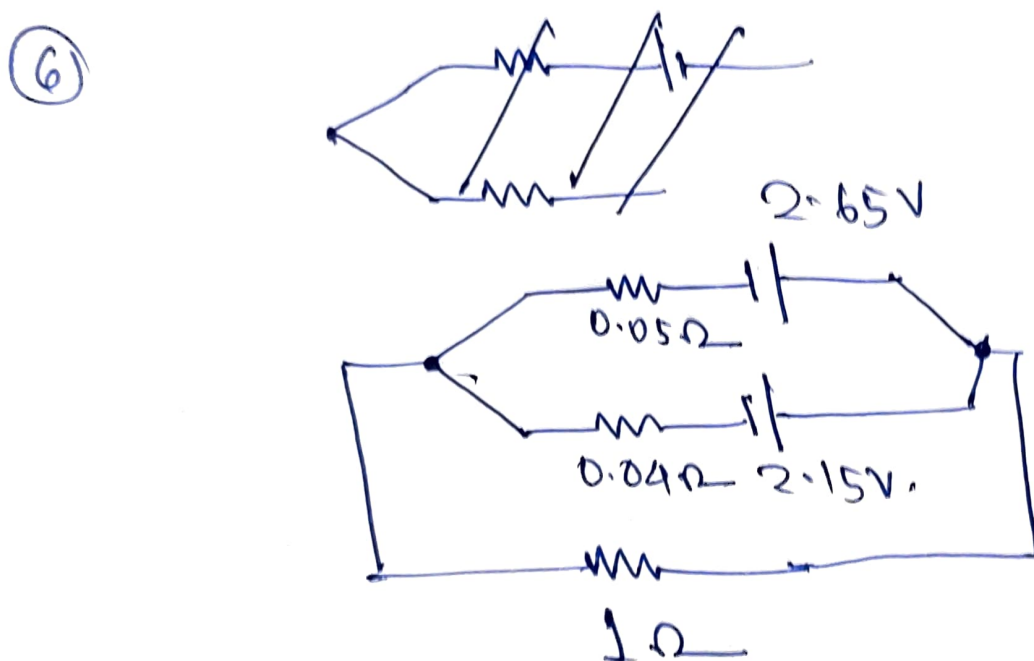Find the current through R using Kirchhoff's law if $R = 12k\Omega$.



Find the current through 1Ω by applying Superposition Principle.

